



Princess Sumaya
University
for Technology

King Abdullah II School of Engineering

EE21221
Electric Circuits (1)
Section #4

Quiz #3
Tuesday 30/11/2021

Name:

Q.1) Calculate i_1 and i_3 if $i_2=1.5$ A in the circuit shown in Figure Q.1. [4-Points]

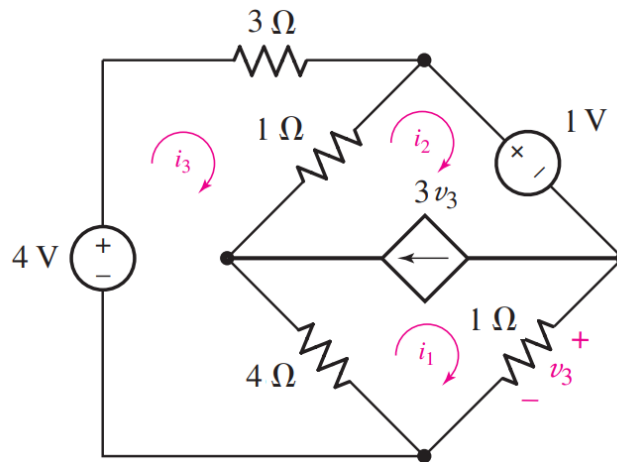


Figure Q.1

Solution:

$i_1 =$

$i_3 =$

Solution :

$$i_2 - i_1 = 3v_3 \rightarrow v_3 = i_1 * (1)$$

$$i_2 - 4i_1 = 0 \dots\dots\dots \textcircled{1}$$


$$\text{mesh } i_3 \rightarrow -4 + 3 * i_3 + 1 * (i_3 - i_2) + 4 * (i_3 - i_1) = 0 \dots\dots\dots \textcircled{2}$$

$$i_1 \text{ \& } i_2 \rightarrow 1 + i_1 * (1) + 4 * (i_1 - i_3) + (i_2 - i_3) * 1 = 0 \dots\dots\dots \textcircled{3}$$


$$i_1 = 0.375 \text{ A}$$

$$i_2 = 1.5 \text{ A}$$

$$i_3 = 0.875 \text{ A}$$

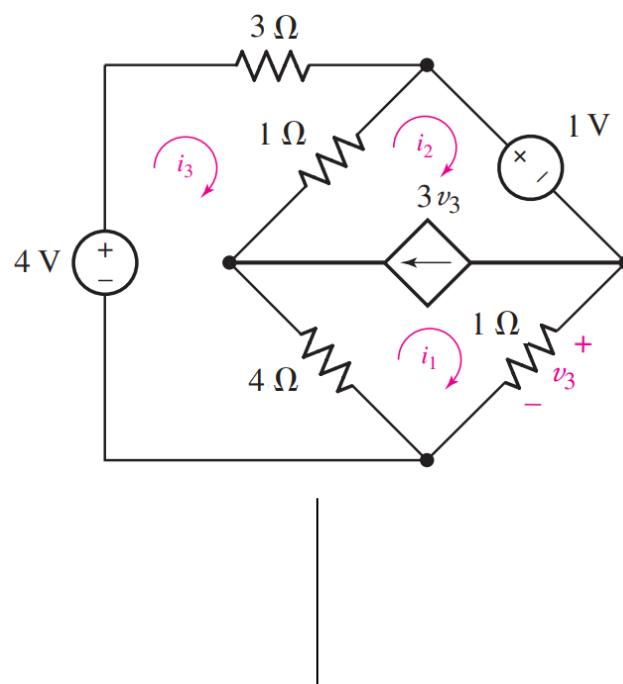

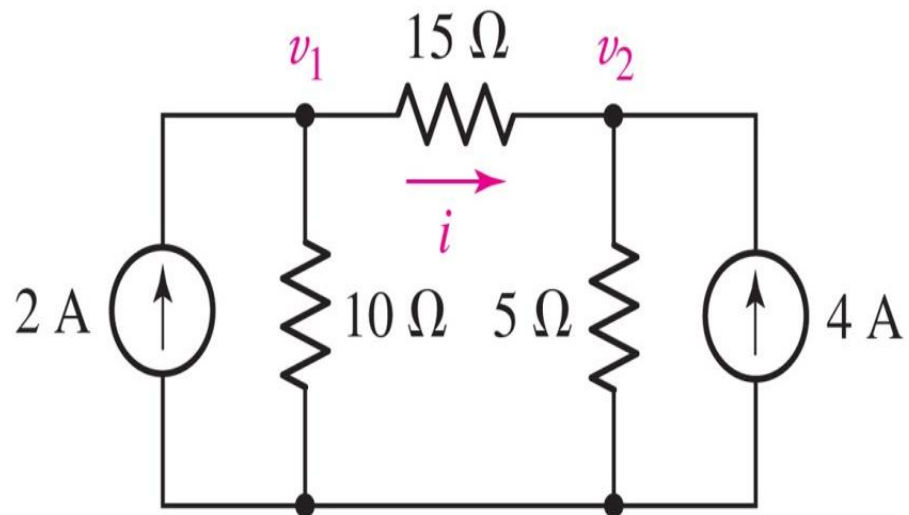Q.2) Find v_1 , v_2 , and i in the circuit shown in Figure Q.2. [6-Points]



Ref.

Figure Q.2

Solution:

$v_1 =$

$v_2 =$

$i =$

EXAMPLE 4.1

Nodal analysis will directly yield numerical values for the nodal voltages v_1 and v_2 , and the desired current is given by $i = (v_1 - v_2)/15$.

Before launching into nodal analysis, however, we first note that no details regarding either the $7\ \Omega$ resistor or the $3\ \Omega$ resistor are of interest. Thus, we may replace their series combination with a $10\ \Omega$ resistor as in Fig. 4.2*b*. The result is a reduction in the number of equations to solve.

Writing an appropriate KCL equation for node 1,

$$2 = \frac{v_1}{10} + \frac{v_1 - v_2}{15} \quad [5]$$

and for node 2,

$$4 = \frac{v_2}{5} + \frac{v_2 - v_1}{15} \quad [6]$$

Rearranging, we obtain

$$5v_1 - 2v_2 = 60$$

and

$$-v_1 + 4v_2 = 60$$

Solving, we find that $v_1 = 20\ \text{V}$ and $v_2 = 20\ \text{V}$ so that $v_1 - v_2 = 0$. In other words, **zero current** is flowing through the $15\ \Omega$ resistor in this circuit!

